

Addition & Subtraction

	2-input Not Gate	2-input And Gate	2-input OR Gate	2-input XOR Gate
Half Adder	-	1	-	1
Full Adder	-	2	1	2
2's Complement	1	8	10	4
Sign Checker	1	3	2	2
Addition	4	29	31	25

Total Number of Addition & Subtraction = 89

Integer division

	Not Gate	2-input And Gate	2-input OR Gate	2-input XOR Gate	2-input NOR Gate
Half Adder	-	1	-	1	0
Full Adder	-	2	1	2	0
Subtractor	4	8	4	8	0
Multibier 4*1	0	4	0	0	0
Comparator	8	23	6	0	4
Others	2	0	10	1	0

For the whole Integer division Circiut:

128- And Gate, 46- OR Gate , 25-XOR Gate, 46-Not Gate,
16-NOR Gate

Total Number of Integer division= 261

BCD to 7 Segment

Not Gate	2-input And Gate	2-input OR Gate
3	9	18

Total Number of BCD to 7 Segment=30

Multiplication

	2-input Not Gate	2-input And Gate	2-input OR Gate	2-input XOR Gate
Half Adder	-	1	-	1
Full Adder	-	2	1	2
Multiplicator	-	36	8	21
Multiplicator with flag	2	37	15	21

For the whole Multiplicator Circiut:

37- And Gate, 15- OR Gate , 21-XOR Gate, 2-Not Gate.

Total Number of Multiplication: 75

Binary To BCD

	2-input Not Gate	2-input And Gate	2-input OR Gate
Shifter	8	18	7
Binary To BCD	56	126	49

For the whole Binary To BCD

126- And Gate, 49- OR Gate , 56-Not Gate.

Total Number of Binary To BCD: 231

.....

ALU

	2-input Not Gate	2-input And Gate	2-input OR Gate	2-input XOR Gate	2-input NOR Gate
MUX	2	8	3		
11 MUX	22	88	33	-	-
Addition & Subtraction	4	29	31	25	-
Multiplicator	2	37	15	21	-
dividor	46	128	46	25	16


For the whole Multiplicator Circiut:

290- And Gate, 128- OR Gate , 71-XOR Gate, 76-Not Gate, 16-NOR Gate


Total Number of ALU = 568

ALU block

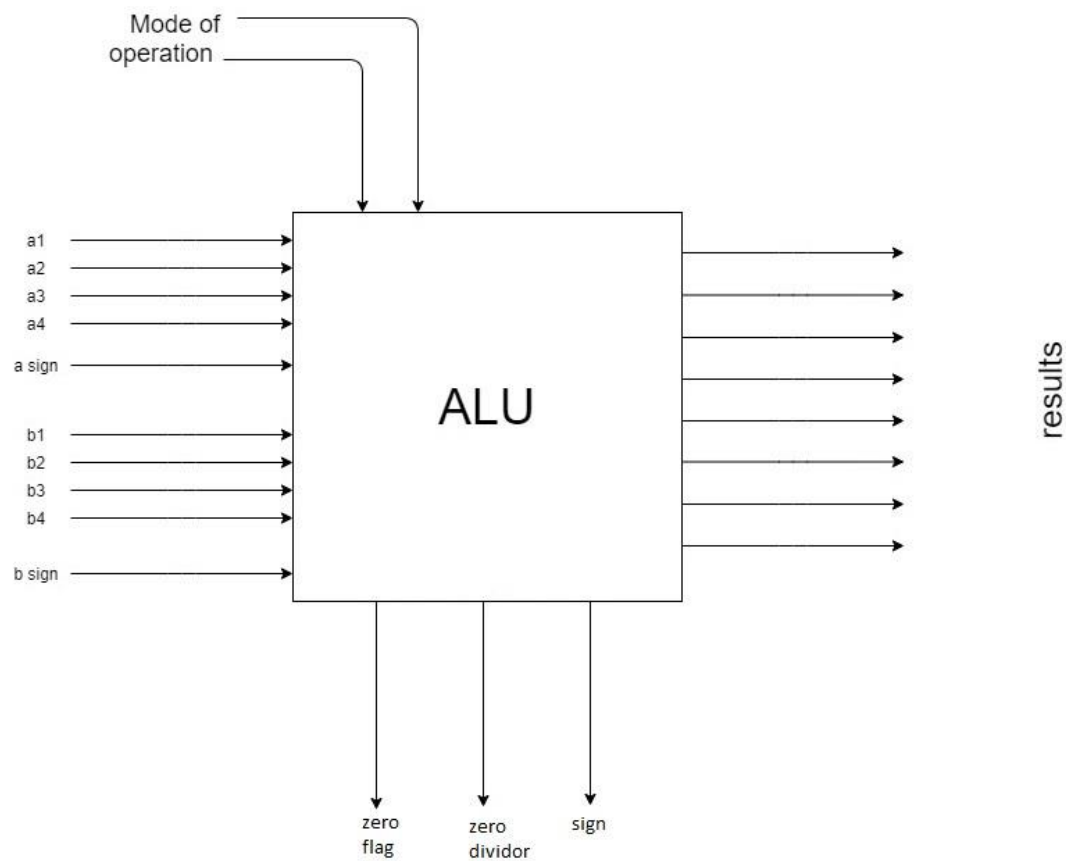
This block take 2 numbers as an inputs (each number in 5 bits) ,and take mode of operation that use 2 bits to determine wich operation will be done







ALU Diagram

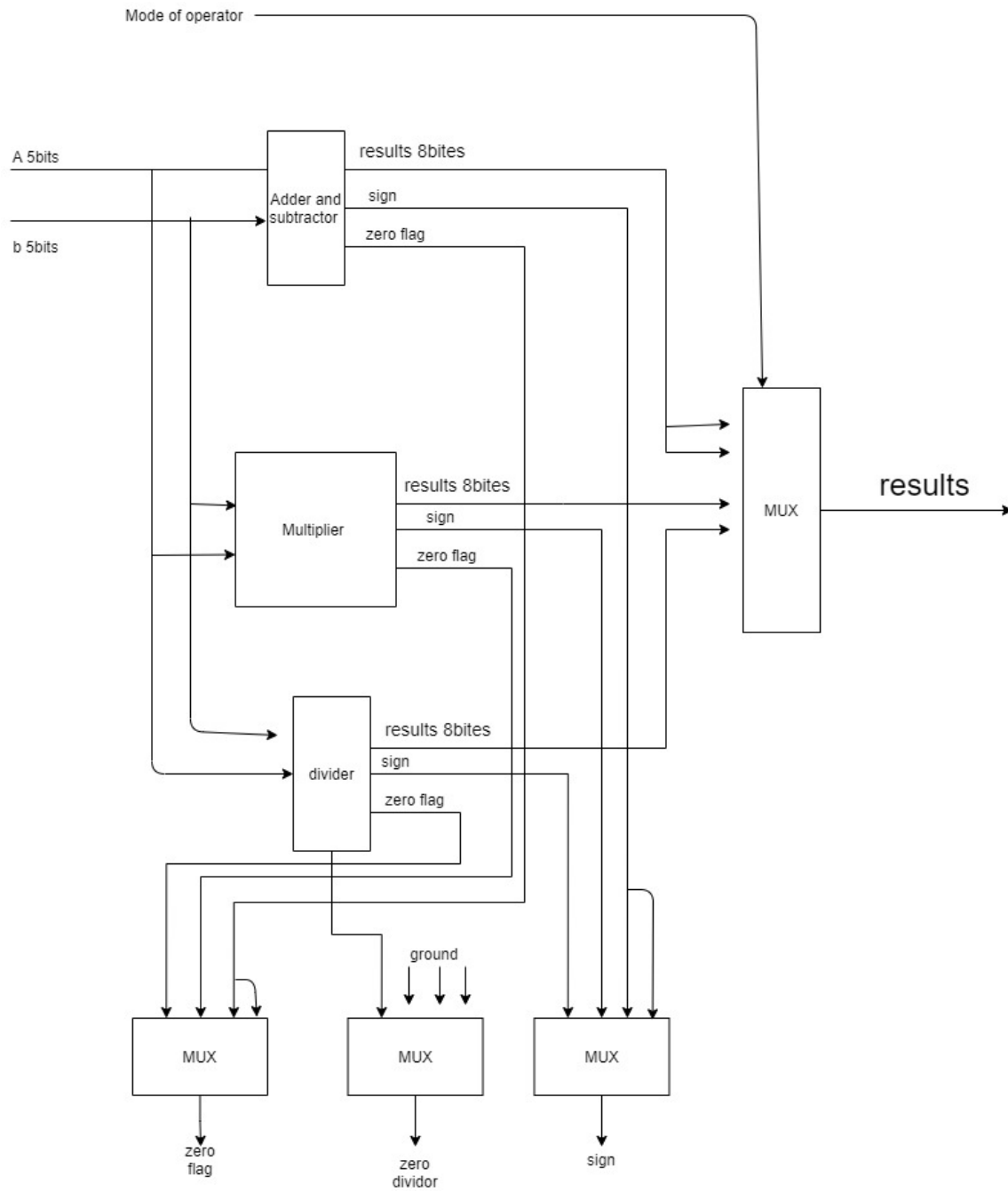



Addition & Subtraction Diagram

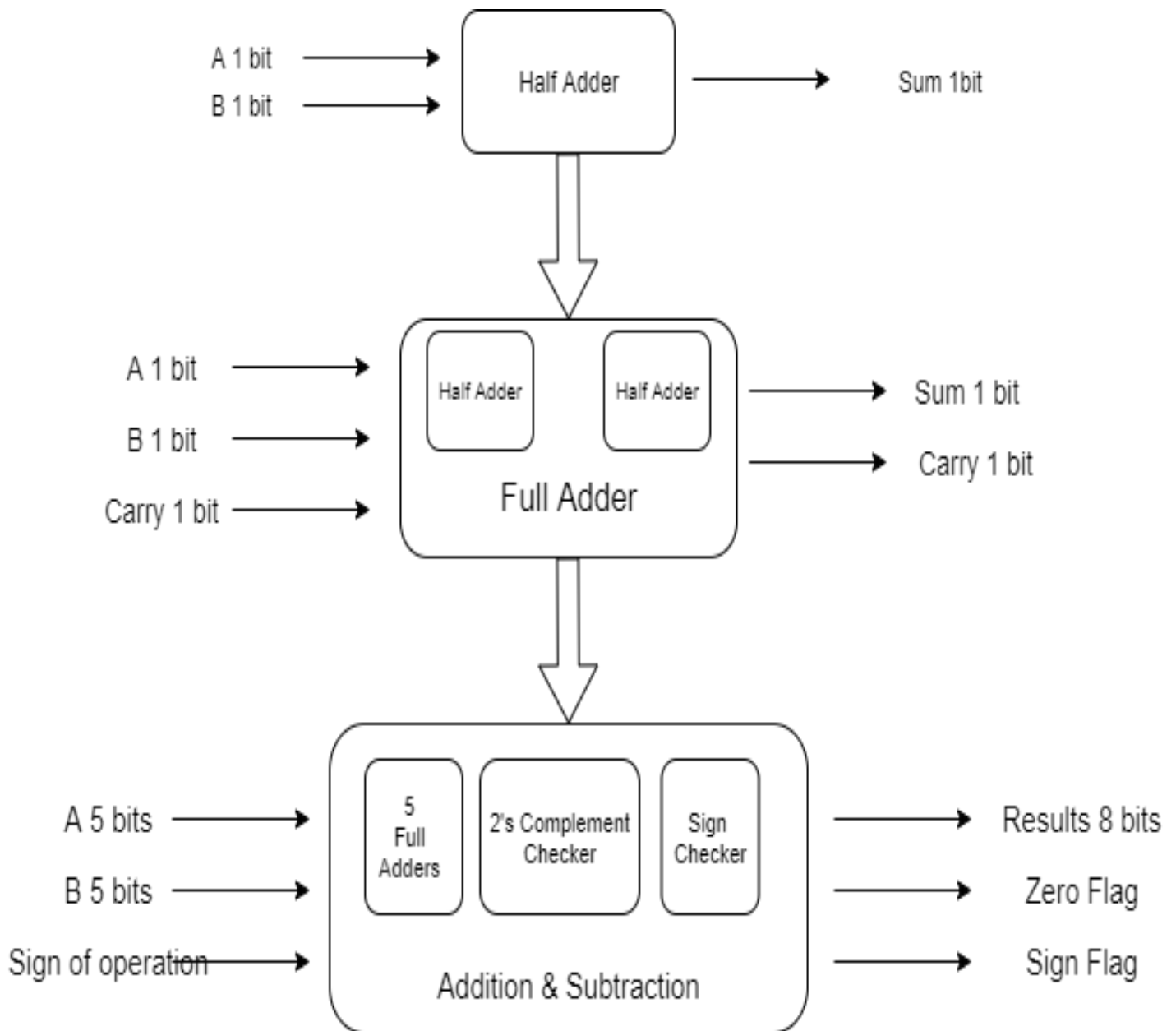

Multiplication

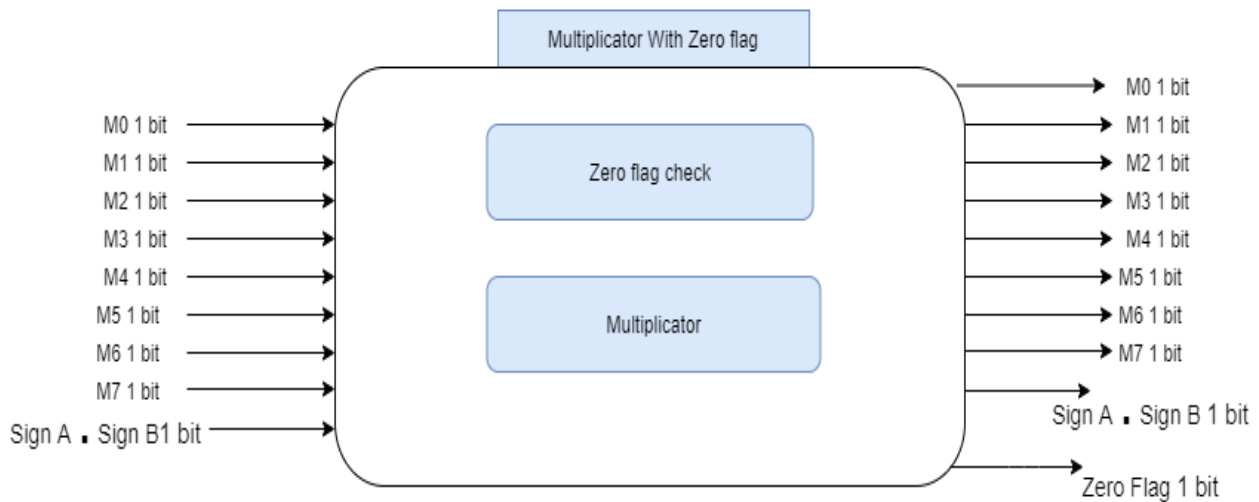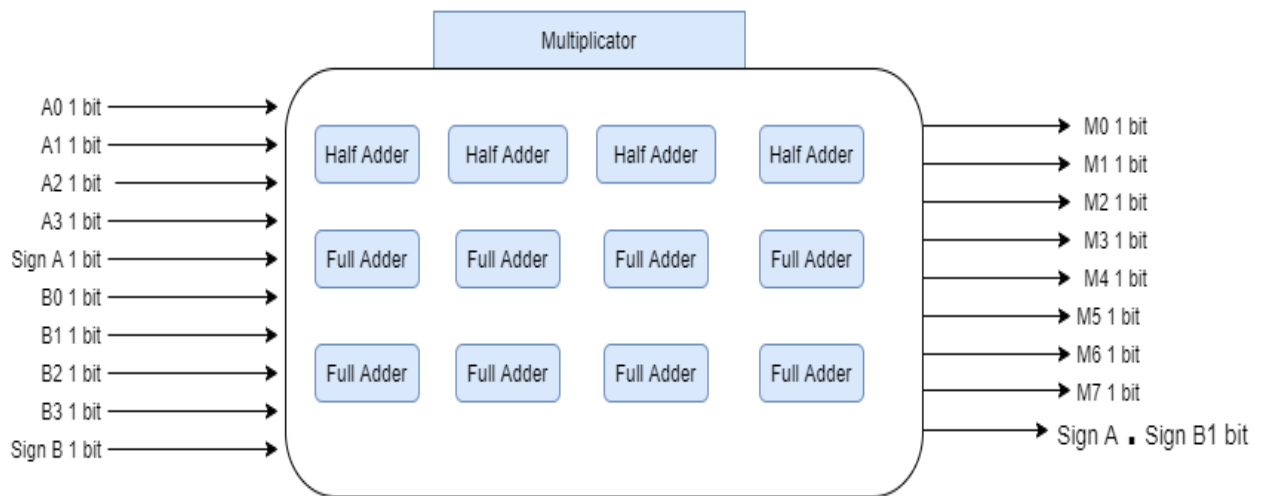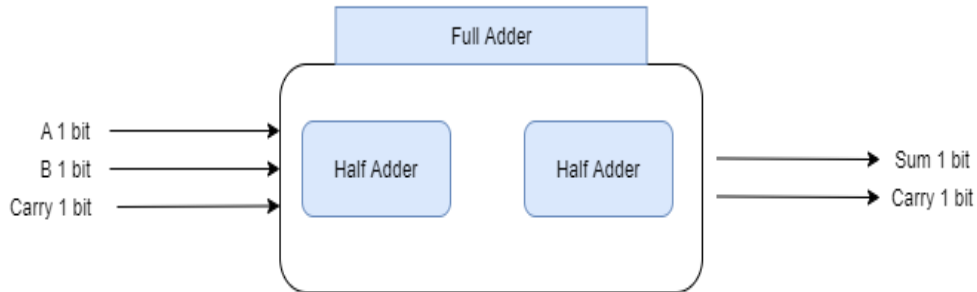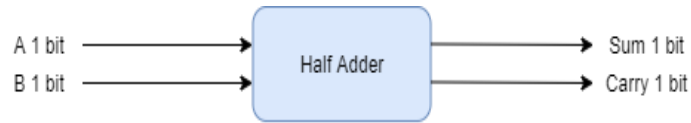

Binary To BCD

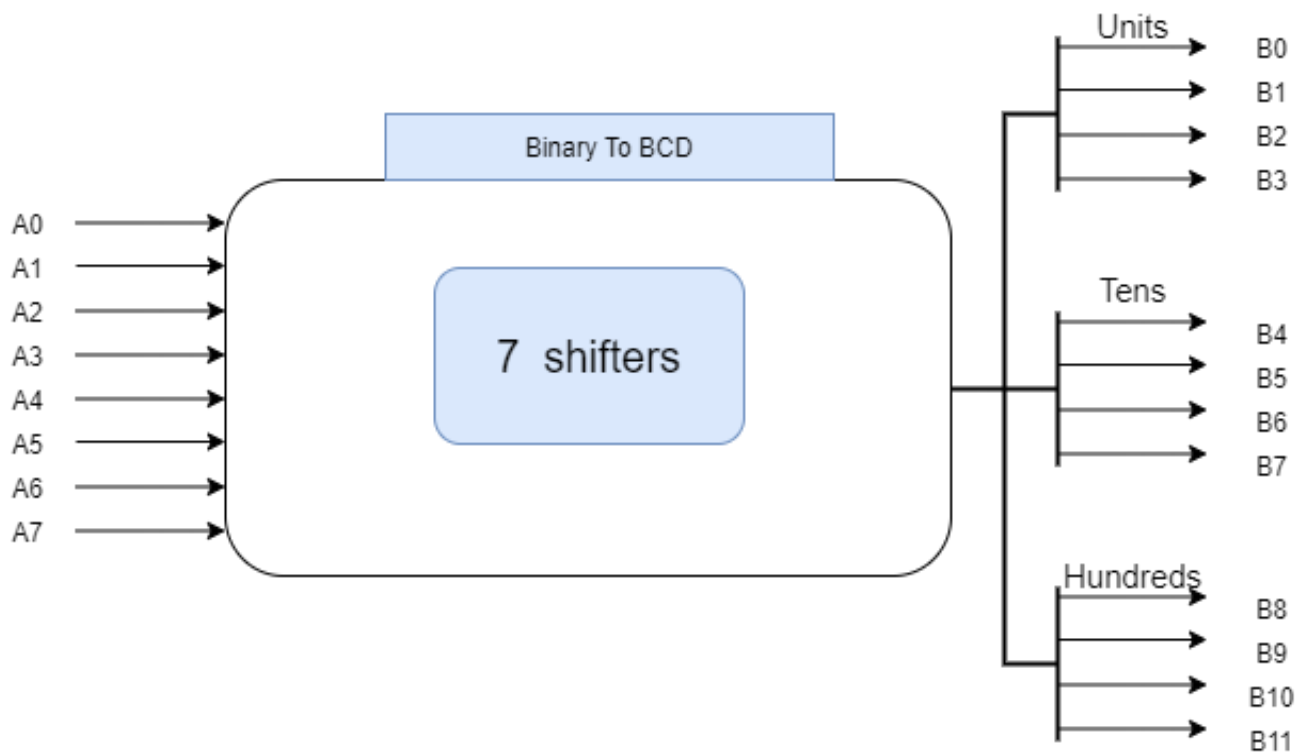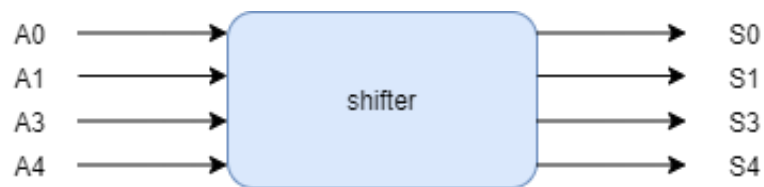

Integer division

integer division

